

# ELC 2137 Lab 3: Adders

Victoria Covey

September 15, 2020

## Summary

In this lab we experimented with carries and sums that are produced in binary adders. We created 3 circuits, all of which came together to make our final 2-bit adder. To prove the circuits and binary calculations the circuit was making were true, the class made separate schematics, wiring diagrams, and truth tables. After this lab, I felt more confident in my ability to read and write a circuit schematic, as well as how to use transistors to make calculations of And and XOR gates.

## Q&A

1. Which gates could we use for combining the carry bits?

We could use AND and XOR gates as we had seen in class.

2. Which of the above should we use and why?

We would want to use the AND gates. The AND gates can be negated in a way that mimics the use of XOR without adding another transistor chip.


# Results

VICTORIA COVEY

ELC 2137

Lab 3. Adders

## Circuit Demonstration Page

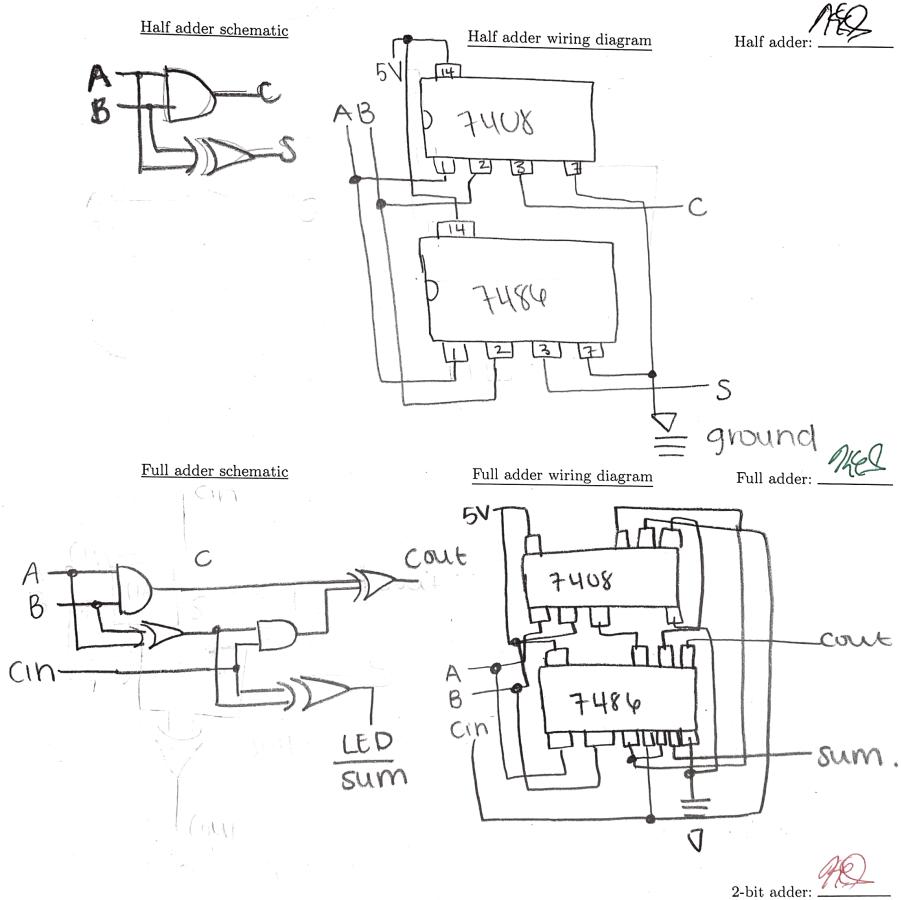

4

fig: Signed Off Circuit Demonstration Page

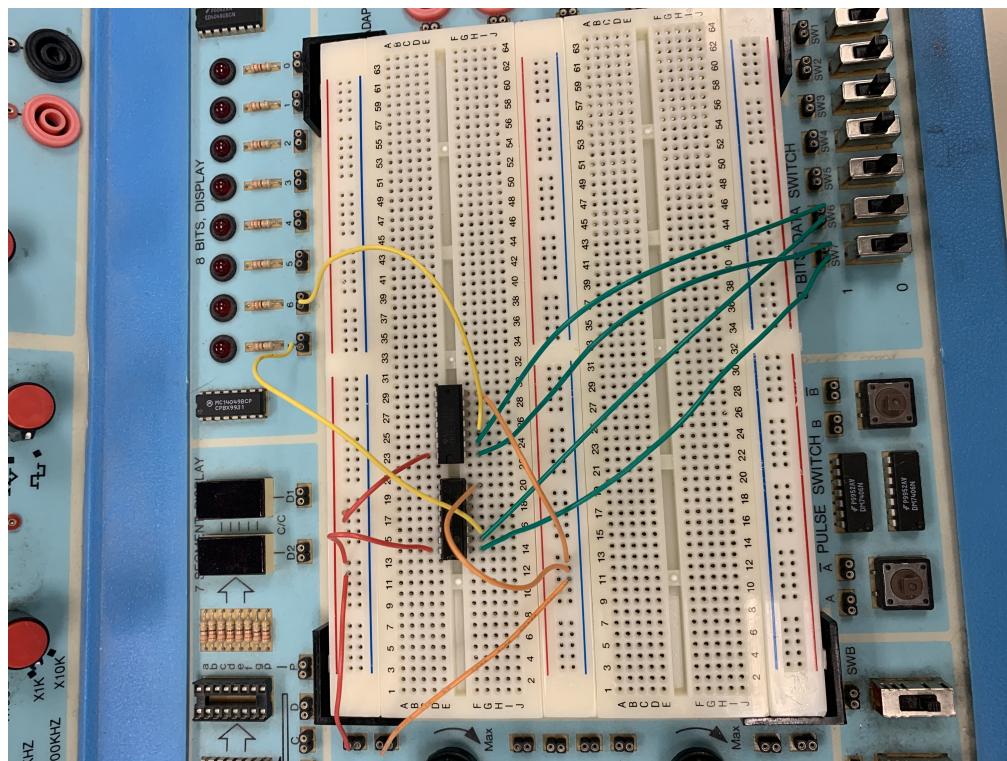


fig: Half Adder Circuit

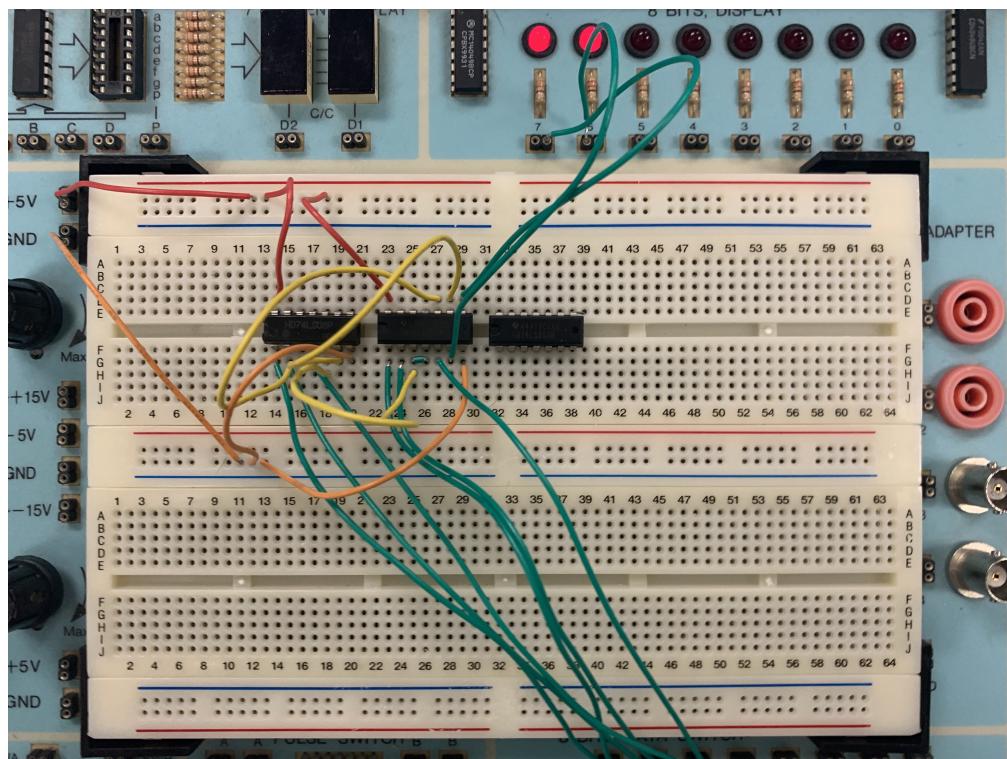


fig: Full Adder Circuit

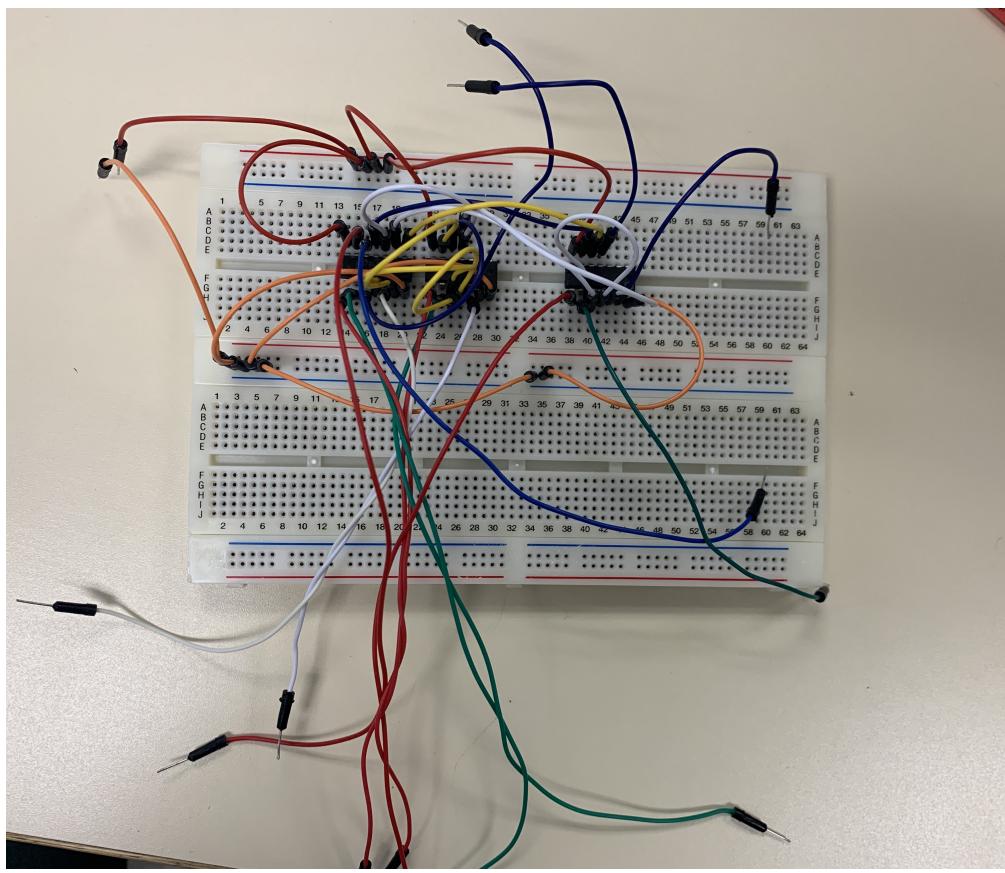


fig: 2 Bit Adder Circuit

Cin	A	B	c1	s1	c2	s2	cout	S
0	0	0	0	0	0	0	0	0
0	0	1	0	1	0	1	0	1
0	1	0	0	1	0	1	0	1
0	1	1	1	0	0	0	1	0
1	0	0	0	0	0	1	0	1
1	0	1	0	1	1	0	1	0
1	1	0	0	1	1	0	1	0
1	1	1	1	0	0	1	1	1

fig: Full Adder Truth Table Showing Half Adders